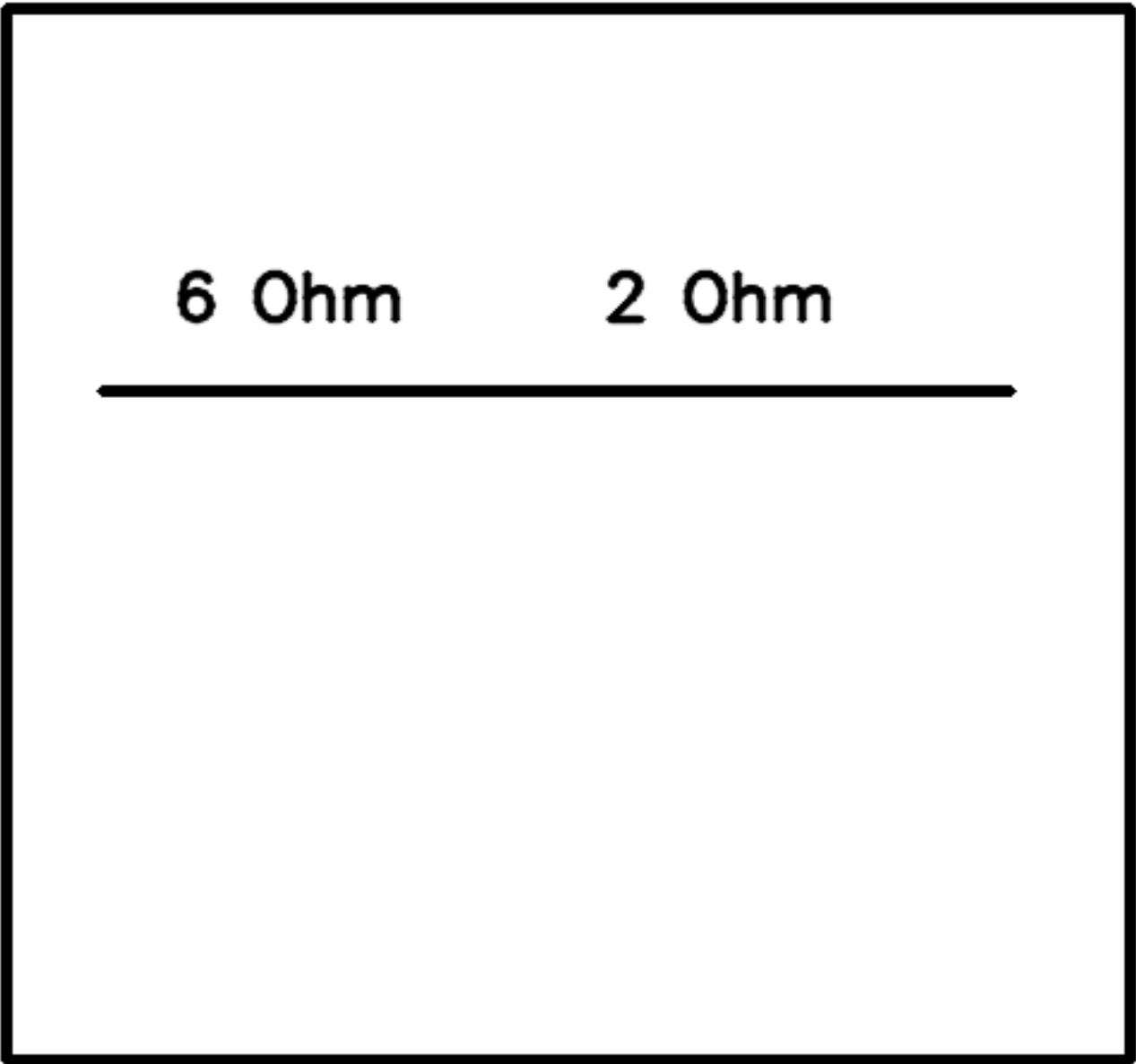


Question 1. What is the total resistance of the circuit shown?



- A. 4 Ohm**
- B. 5 Ohm**
- C. 6 Ohm**
- D. 7 Ohm**